



SMART TEST SERIES

www.notespk.com : info@notespk.com

Name:		Subject:	Physics-12
Roll # :		Unit(s):	13,
Class:	Inter Part-II	Test:	Type 8 - Short Test (No Choice) - Marks=30
Date:		Time:	

Q.1 Circle the Correct Answers.

(6x1=6)

- The heat produced by the passage of current through a resistor is:
(A) $H = I^2 R t$ (B) $H = I R^2 t$ (C) $H = \frac{I}{R t}$ (D) $H = \frac{I^2}{R t}$
- Magnetic effect of current is used in:
(A) Toaster (B) Electric motor (C) Electric iron (D) D.C battery
- Heat generated by a 50 watt bulb in one hour is:
(A) 36000 J (B) 48000 J (C) 18000 J (D) 180000 J
- For ohmic device the graph between V and I is:
(A) A straight line (B) Curve (C) Hyperbola (D) Parabola
- Temperature coefficient of resistance(α) is equal:
(A) $\frac{R_t + R_o}{R_o \Delta t}$ (B) $\frac{R_o - R_t}{R_o \Delta t}$ (C) $\frac{R_t - R_o}{R_o \Delta t}$ (D) None of these
- Siemen is the unit of:
(A) Resistivity (B) Resistance (C) Conductivity (D) Conductance

Q.2 Write short answers of the following questions.

(8x2=16)

- What is unit of electric current? Define it.
- A potential difference is applied across the ends of a copper wire. What is the effect on the drift velocity of free electrons by a) increasing the potential difference b) decreasing the length and temperature of the wire?
- What are the difficulties in testing whether the filament of a lighted bulb obeys Ohm's Law?
- Define temperature coefficient of resistance. Give its unit.
- Give colour code of carbon resistor.
- Explain why the terminal potential difference of battery decreases when the current drawn from it is increased?
- Write down the rules for finding the potential changes along a circuit.
- Why we prefer potentiometer in place of voltmeter for measuring potential difference?

NOTE: Attempt the long question.

(5+3=8)

- Define electric power. Also explain how power is dissipated in resistor?
- How many electrons pass through a electric bulb in one minute if 300 mA current is passing through it?